
Indian Institute of Technology Jodhpur
Department of Electrical Engineering
End Term Examination
[EEL2020/CSL2070] Digital Design


MM: 60
Time: 2 hours

April 28, 2022

1. A car parking system employs sensors to detect the occupancy of a parking area. Design the hardware to implement the following minimum functionalities.
 - Space of parking 12 cars with sensors S1 to S12.
 - In each parking slot, the sensor gives output 1 when a car is parked, and 0 when the parking area is empty.
 - An LED indicator outside to show whether the parking is full (RED LIGHT) or vacant (GREEN LIGHT).
 - A counter to show the number of vacant parking slots.

Write a Verilog Code for the design. Give a clear block diagram to explain the inputs, outputs and various parts of the code. [Do not write a code for display unit. It is understood that the counter output will go to display unit. Only show this in the block diagram] [10]

 2. Reduce the following state diagram [2]




Implement the minimum design using

- a) D flip-flops [4]
- b) J-K flip-flops [4]
- c) T-flip-flops [4]
- d) Analyze the design of (b) to show unused states in the final design. [3]

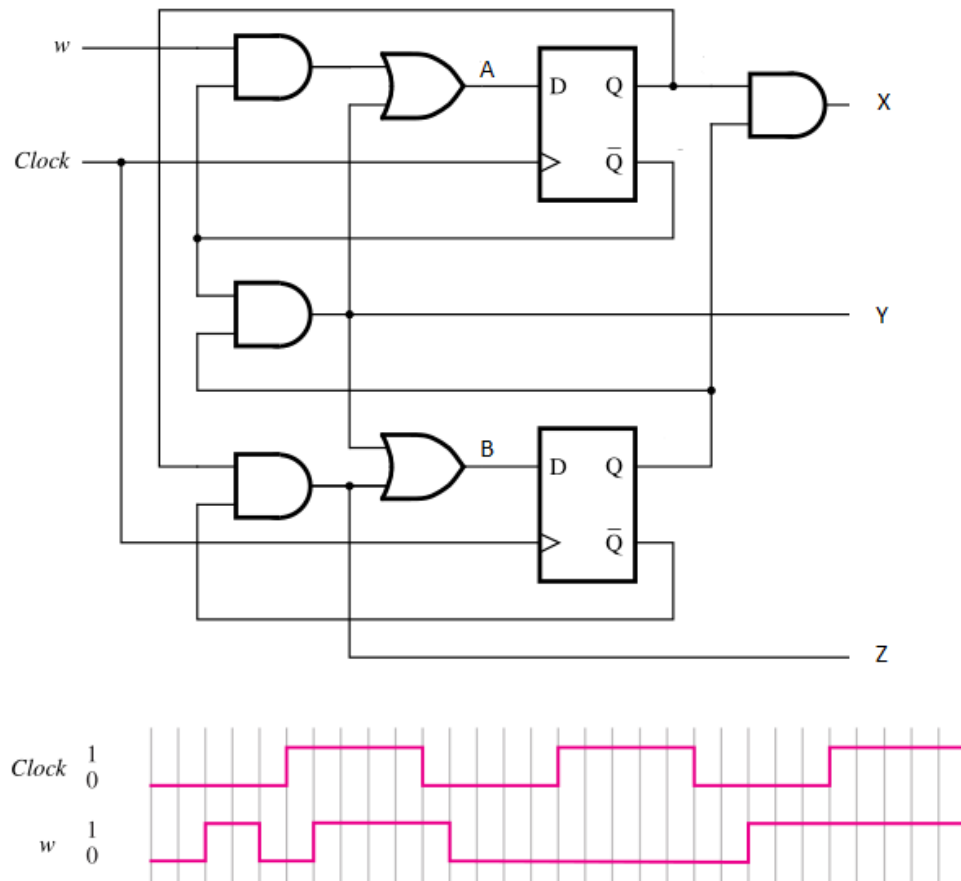3. A circuit is shown below with the following timing parameters for individual components.

- AND Gate propagation delay: 3 ns
- OR Gate propagation delay: 2 ns

The input and clock signals are also shown in the figure, with markings at 1 ns.



- Provide the sequences for A, B, X, Y, Z (with 1 ns timing). Assume that the flip-flops are ideal, and in reset state initially. [2 × 5]
- Suppose, the following timing parameters are available for the D flip-flops.
 - Setup time [Data must be available at D before the active edge]: 1 ns.
 - Hold time [Data must be available at D after the active edge]: 1 ns.
 - Propagation delay [Data is available at Q and Q' after the active edge of clock]: 4 ns.

What is the maximum frequency at which this circuit can operate. Justify your answer. [5].

-
4. A combinational circuit is given by $Z = AC' + A'C + BC' + AB'$
- a) Show the internal structure/connections of the LUT, and SRAM data for implementing Z with
 - i. 2 input LUTs [3]
 - ii. 3 input LUTs [3]
 - b) Show the implementation (programming) of Z on FPGA with 2 input LUTs of part (a). [6]
5. A synchronous counter is desired that provides a 3 bit gray code output sequence with the following properties.
- State 000,111 does not occur. These are skipped in the sequence.
 - States 001,010,100 stays for 1 clock cycle.
 - States 011,101,110 stays for 2 clock cycles.
- a) Provide the state diagram for the design. [3]
 - b) Provide the state table for the design. [3]