


CSL2070 Digital Design

Lab Report

Roll Number	B20CS029
Name	Kulkarni Tanmay Shreevallabh
Lab number	Lab5
Experiment Title	<ul style="list-style-type: none"> Barrel Shifter 32 Bit ALU 4x2 Priority Encoder using a) Casex Statements b) For loop Behavioral Code for implementing a) BCD adder and subtractor b) Multiply by 5 circuit

Barrel Shifter

Circuit Diagram

 

Code

```

module barrel_shifter(selection,w,y);
input [1:0]selection;
input [3:0]w;
output [3:0]y;
assign y[3]=(!selection[0])&(!selection[1])&(w[3])|(selection[0])&(!selection[1])&(w[0])|(!selection[0])&(selection[1])&(w[1])|(selection[0])&(selection[1])&(w[2]);
assign y[2]=(!selection[0])&(!selection[1])&(w[2])|(selection[0])&(!selection[1])&(w[3])|(!selection[0])&(selection[1])&(w[0])|(selection[0])&(selection[1])&(w[1]);
assign y[1]=(!selection[0])&(!selection[1])&(w[1])|(selection[0])&(!selection[1])&(w[2])|(!selection[0])&(selection[1])&(w[3])|(selection[0])&(selection[1])&(w[0]);
assign y[0]=(!selection[0])&(!selection[1])&(w[0])|(selection[0])&(!selection[1])&(w[1])|(!selection[0])&(selection[1])&(w[2])|(selection[0])&(selection[1])&(w[3]);
endmodule


```

Code for Test Bench

```
module test_barrel_shifter;
reg [1:0]selection;
reg [3:0]w;
wire [3:0]y;

barrel_shifter(selection,w,y);
initial
begin
    w = 4'b1010;
    selection = 2'b00;
end
always #20 selection = selection + 1'b1;
always #80 w = w + 1'b1;
initial #1000 $finish;
endmodule
```

Waveform

 

32 Bit ALU

Circuit Diagram

Operation	Input	32 bit Output
Clear	000	0
Addition	001	A + B
Subtraction	010	A - B
A * 2	011	Left shift
A / 2	100	Right Shift
A AND B	101	A & B
A OR B	110	A B
A XOR B	111	A ^ B

1

Code

```
module alu(a,b,operation,f);  
parameter n = 32;  
input [n-1:0]a,b;  
output reg [n-1:0]f;  
input [2:0] operation;  
always @ (operation)  
begin  
case(operation)  
0:f=0;  
1:f=a+b;  
2:f=a-b;  
3:f=a<<1;  
4:f=a>>1;  
5:f=a&b;  
6:f=a|b;  
7:f=a^b;  
endcase  
end  
endmodule
```

Code for Test- Bench

```
module test_alu;
parameter n = 32;
reg [2:0] operations;
reg [n-1:0] a, b;
wire [n-1:0] f;
alu A(a, b, operations, f);
initial
begin
    a=32'b00000000000000000000000000001011; // a=11
    b=32'b00000000000000000000000000001000; // b=8
    operations=3'b000;
end
always #10 operations=operations+1'b1;
initial #80 $finish;
endmodule
```

Waveform



Behavioral Code for Implementing

a) Adder and Subtractor unit


Code

```
module bcd_adder_subtractor(a, b, op, t, o, sign);
// op=1 stands for addition and op=0 stands for subtraction
// sign=0 means positive and sign=1 means negative
input [3:0] a, b;
input op;
reg [4:0] f;
output [3:0] o;
output [1:0] t;
output reg sign;
always @ (op)
begin
if (op)
begin
sign=0;
f=a+b;
end
else
begin
if (a>=b)
begin
sign=0;
f=a-b;
end
else
begin
sign=1;
f=b-a;
end
end
end
bcd_conv bc(f,t,o);
endmodule
```

Code for Test- Bench

```
module test_bcd_adder_subtractor();
reg [3:0] a, b;
reg op;
wire [3:0] o;
wire [1:0] t;
wire sign;
bcd_adder_subtractor bas(a,b,op,t,o,sign);
initial
begin
a=4'b1010;
b=4'b1111;
op=1'b1;
#20
op=1'b0;
#20
a=4'b1101;
b=4'b1011;
op=1'b1;
#20
op=1'b0;
end
initial #80 $finish;
endmodule
```

Waveform

 

b) FMultiplierX5


Code

```
module multiplierX5(a, f);  
input [3:0] a;  
output reg [6:0] f;  
always @ (a)  
begin  
f=((a<<1)<<1)+a;  
end  
endmodule
```

Code for Test- Bench

```
module test_multiplierX5();  
reg [3:0] a;  
wire [6:0] f;  
multiplierX5 m(a,f);  
initial  
begin  
a=4'b0000;  
end  
always #10 a=a+1'b1;  
initial #1000 $finish;  
endmodule
```

Waveform

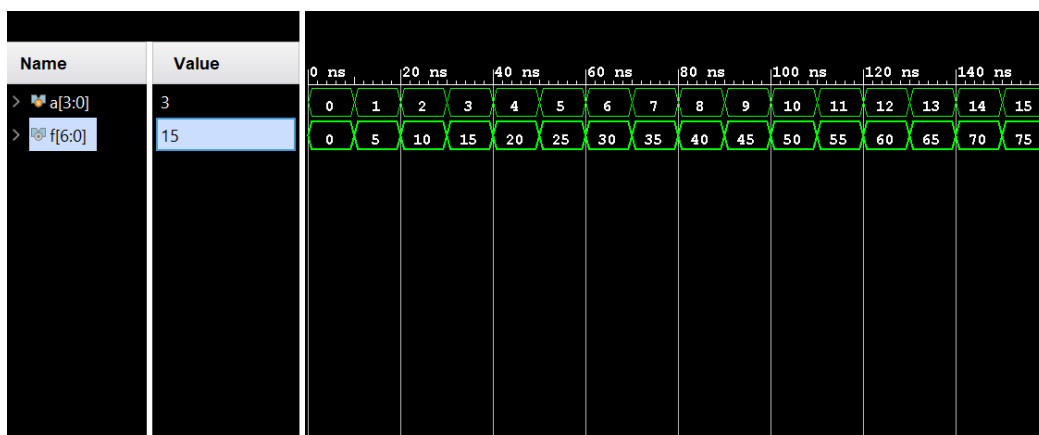

Priority Encoders

b) Casex Statements

Code

```
module priority_encoder_a(d,x,v);
input [3:0]d;
output reg[1:0]x;
output reg v;
always @(d)
begin
v=1;
casex(d)
4'b1XXX: x=2'b11;
4'b01XX: x=2'b10;
4'b001X: x=2'b01;
4'b0001: x=2'b00;
default:
begin
v=0;
x=2'b00;
end
endcase
end
endmodule
```

Code for Test- Bench

```
module test_priority_encoder_a;
reg [3:0] d;
wire [1:0] x;
wire v;
priority_encoder_a pea(d, x, v);
initial
begin
d=4'b0000;
end
always #10 d=d+1'b1;
initial #160 $finish;
endmodule
```

Waveform



Priority Encoders

a) For Loop

Code

```

module priority_encoder_b(d,x,v);
input [3:0] d;
output reg [1:0] x;
output reg v;
integer k;
always @ (d)
begin
x=2'bXX;
v=0;
for (k=0; k<4; k=k+1)
if (d[k])
begin
x=k;
v=1;
end
end
endmodule

```

Code for Test- Bench

```
module test_priority_encoder_b;
  reg [3:0] d;
  wire [1:0] x;
  wire v;
  priority_encoder_b peb(d, x, v);
  initial|
begin
  d=4'b0000;
end
always #10 d=d+1'b1;
initial #160 $finish;
endmodule
```

Waveform

